

# Resistance and Ohm's Law Questions for GCSE Physics (ANSWERS)



1. What are the units for resistance?

*Ohms (or  $\Omega$ )*

2. What is Ohm's law in equation form?

*$V = IR$  (or  $I = V/R$  or  $R = V/I$ )*

3. What is Ohm's law in words?

*The current through a component is proportional to the voltage across it at a constant temperature.*

4. A resistor has a potential difference of 12 V across it and a current of 3 A flowing through it. Calculate the resistance.

*$R = V/I = 12/3 = 4\Omega$*

5. A resistor has a resistance of 5  $\Omega$  and a current of 2 A flowing through it. Calculate the voltage across it.

*$V = IR = 2 \times 5 = 10V$*



6. A lamp has a resistance of  $20\ \Omega$  and a potential difference of  $10\ \text{V}$  across it. Calculate the current flowing through it.

---

$$I = V/R \quad = 10/20 \quad = 0.5\ \text{A}$$

---

7. A component has a resistance of  $8\ \Omega$  and a voltage of  $24\ \text{V}$  across it. Calculate the current.

---

$$I = V/R \quad = 24/8 \quad = 3\ \text{A}$$

---

8. A current of  $0.5\ \text{A}$  flows through a resistor when the voltage across it is  $6\ \text{V}$ . Calculate the resistance.

---

$$R = V/I \quad = 6/0.5 \quad = 12\ \Omega$$

---

9. Three resistors of  $10\ \Omega$ ,  $15\ \Omega$  and  $5\ \Omega$  are connected in series. Calculate the total resistance.

---

$$R = 10 + 15 + 5 = 30\ \Omega$$

---

10. Two resistors of  $40\ \Omega$  and  $60\ \Omega$  are connected in series to a  $10\ \text{V}$  battery.  
a) Calculate the total resistance.      b) Calculate the current in the circuit.

---

$$\text{a) } 40 + 60 = 30\ \Omega$$

---

$$\text{b) } I = V/R \quad = 10/100 \quad = 0.1\ \text{A}$$

---



11. A circuit contains resistors of  $25\ \Omega$ ,  $35\ \Omega$  and  $40\ \Omega$  connected in series to a  $20\ \text{V}$  battery.  
a) Calculate the total resistance.    b) Calculate the current in the circuit.

---

$$\text{a) } 25 + 35 + 40 = 100\ \Omega$$

---

$$\text{b) } I = V/R \quad = 20 / 100 \quad = 0.2\ \text{A}$$

---

12. A resistor has a resistance of  $12\ \Omega$  and carries a current of  $0.5\ \text{A}$ . Calculate the voltage across it.

---

$$V = I R \quad = 0.5 \times 12 \quad = 6\ \text{V}$$

---

13. What happens to the resistance of a wire if its length is doubled? Explain your answer.

---

*If length is doubled then the resistance is doubled*

---

*because it is twice as difficult for the charges to pass through the wire*

---

*or because resistance is proportional to length*

---

14. Two resistors of  $30\ \Omega$  and  $50\ \Omega$  are connected in series with a battery. The current flowing in the circuit is  $0.25\ \text{A}$ . What is the voltage across the battery?

---

$$V = I R \quad = 0.25 \times (30 + 50) \quad = 0.25 \times 80 \quad = 20\ \text{V}$$

---

15. What happens to the resistance of a wire if it is made thicker?

---

*As the thickness increases, the resistance decreases*

---

*because there is more area for the charges to pass through.*

---

