

Resistance and Ohm's Law Questions for GCSE Physics



1. What are the units for resistance?

2. What is Ohm's law in equation form?

3. What is Ohm's law in words?

4. A resistor has a potential difference of 12 V across it and a current of 3 A flowing through it. Calculate the resistance.

5. A resistor has a resistance of 5 Ω and a current of 2 A flowing through it. Calculate the voltage across it.

6. A lamp has a resistance of 20Ω and a potential difference of 10 V across it. Calculate the current flowing through it.

7. A component has a resistance of 8Ω and a voltage of 24 V across it. Calculate the current.

8. A current of 0.5 A flows through a resistor when the voltage across it is 6 V . Calculate the resistance.

9. Three resistors of 10Ω , 15Ω and 5Ω are connected in series. Calculate the total resistance.

10. Two resistors of 40Ω and 60Ω are connected in series to a 10 V battery.
a) Calculate the total resistance. b) Calculate the current in the circuit.



11. A circuit contains resistors of $25\ \Omega$, $35\ \Omega$ and $40\ \Omega$ connected in series to a $20\ \text{V}$ battery.
a) Calculate the total resistance. b) Calculate the current in the circuit.

12. A resistor has a resistance of $12\ \Omega$ and carries a current of $0.5\ \text{A}$. Calculate the voltage across it.

13. What happens to the resistance of a wire if its length is doubled? Explain your answer.

14. Two resistors of $30\ \Omega$ and $50\ \Omega$ are connected in series with a battery. The current flowing in the circuit is $0.25\ \text{A}$. What is the voltage across the battery?

15. What happens to the resistance of a wire if it is made thicker?

