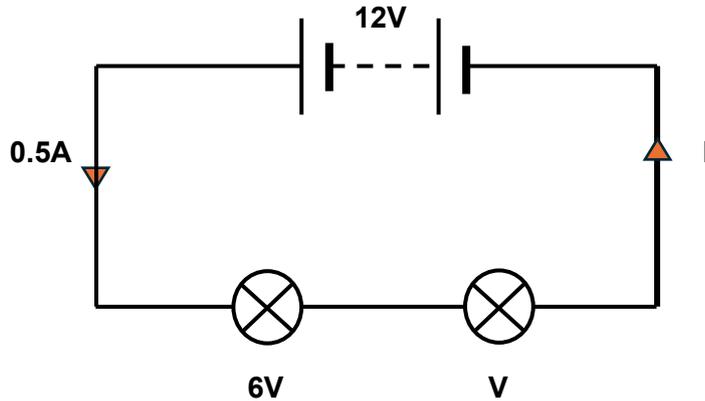


Series and Parallel Circuit Questions for GCSE Physics (ANSWERS)


1. What are the values of V and I in this diagram?



$I = \dots 0.5\text{A} \dots$ (the current is the same everywhere in series)

$$V = \dots 12 - 6 = 6\text{V} \dots$$

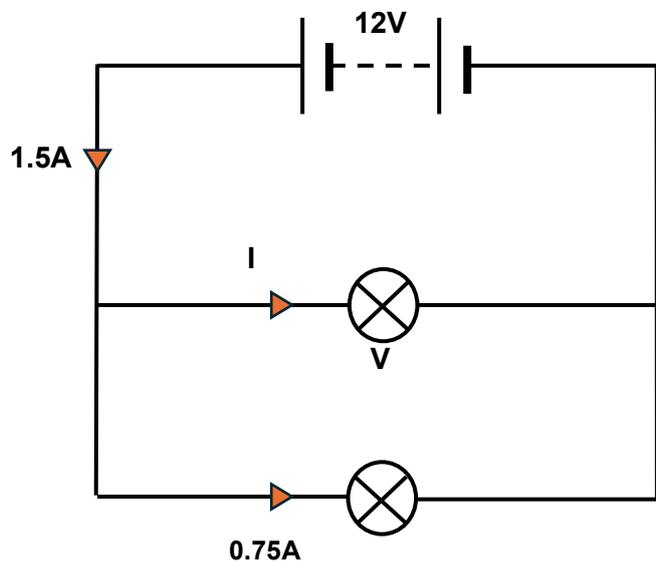
2. What are the values of V and I in this diagram?



$$I = \dots 1.5 - 0.75 = 0.75\text{A} \dots$$

$$V = \dots 12\text{V} \dots$$

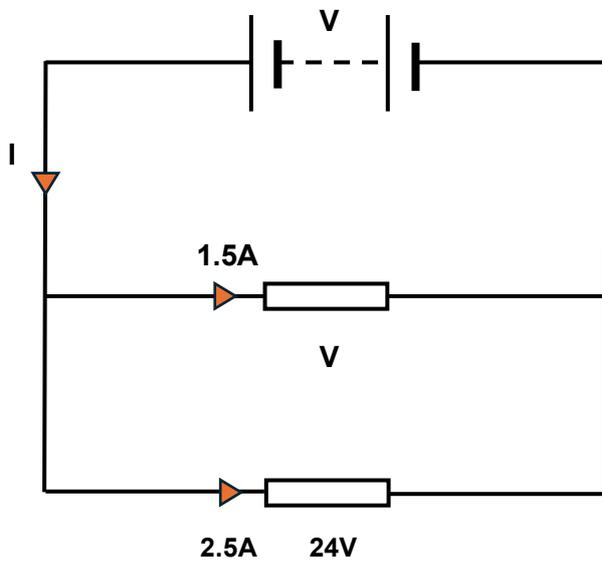
3. This diagram shows 2 different resistors in parallel. What are the values of current I , and voltage V ?



$$I = \dots 1.5 + 2.5 = \mathbf{4A} \dots$$

$$V = \dots \mathbf{24V} \dots$$

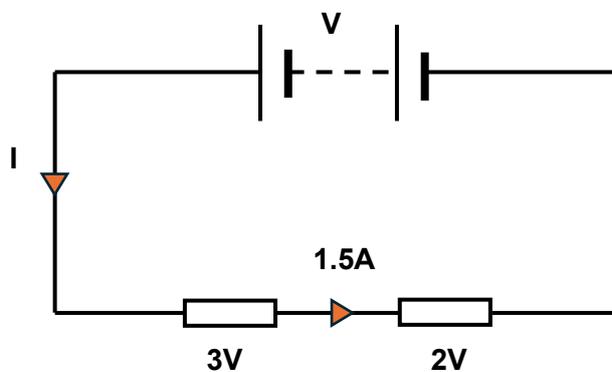
4. This diagram shows 2 different resistors in series. What are the values of current I , and voltage V ?



$$I = \dots \mathbf{1.5A} \dots$$


$$V = \dots 3 + 2 = \mathbf{5V} \dots$$

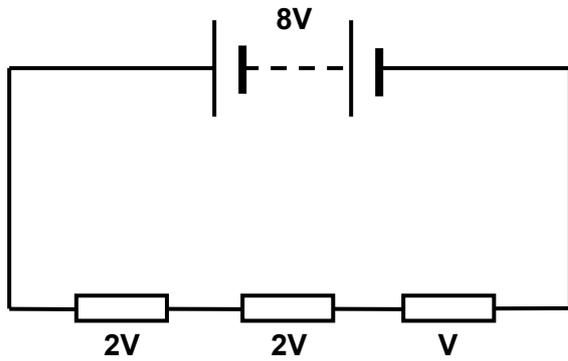5. These resistors may have different values. What is the value of V ?




$$V = \dots 8 - 2 - 2 = 4V \dots$$

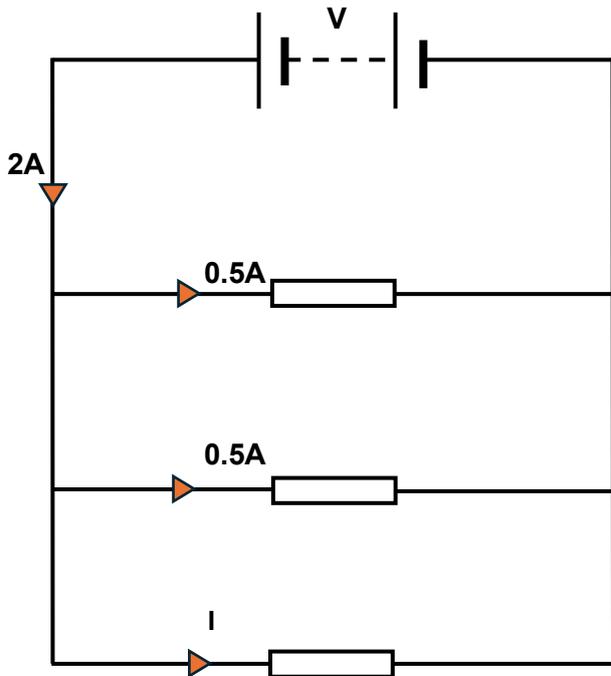6. These resistors may have different values. What is the value of I ?



$$I = \dots 2 - 0.5 - 0.5 = 1A \dots$$

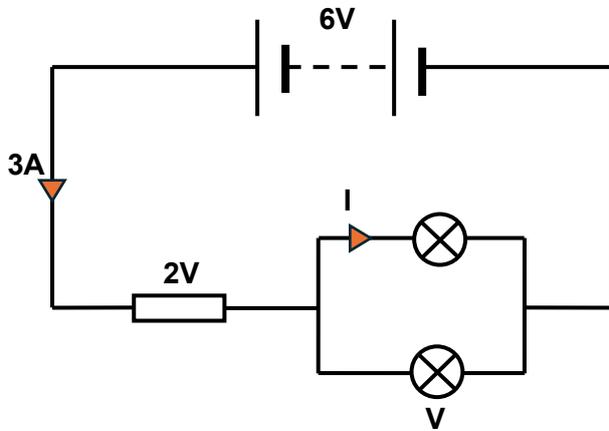
7. The two lamps in this diagram are identical. What are the values of V and I ?



(3A splits in two)
 $I = \dots 1.5\text{A} \dots$

$V = \dots 6\text{V} - 2\text{V} = 4\text{V} \dots$

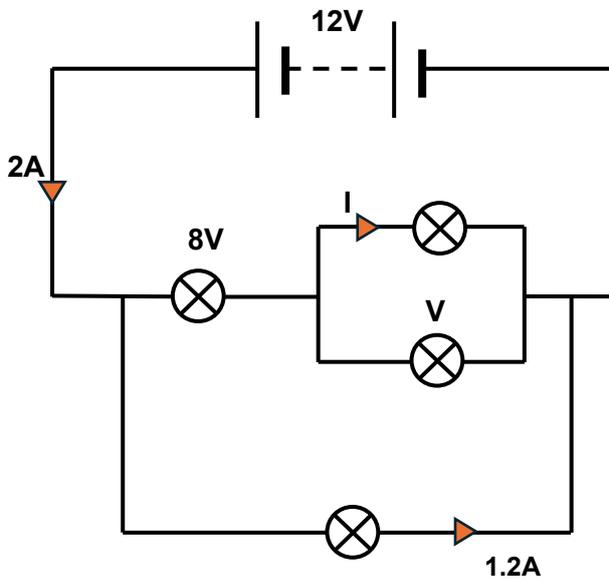8. All the lamps are identical in this circuit. What are the values of I and V ?



($2\text{A} - 1.2\text{A} = 0.8\text{A}$ which then splits)

$I = \dots 0.4\text{A} \dots$

$V = \dots 12\text{V} - 8\text{V} = 4\text{V} \dots$