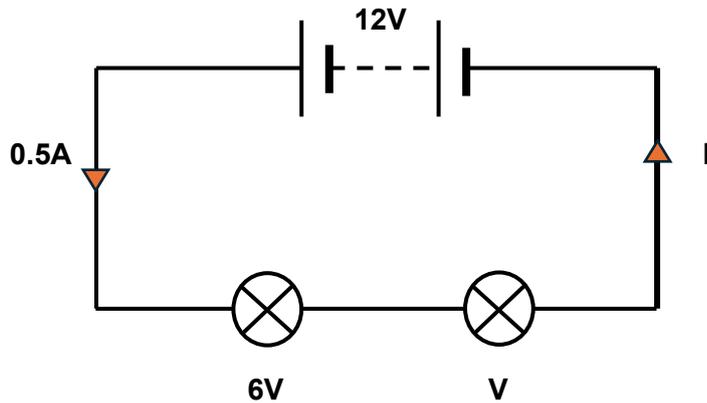


Series and Parallel Circuit Questions for GCSE Physics


1. What are the values of V and I in this diagram?



$I = \dots\dots\dots$

$V = \dots\dots\dots$

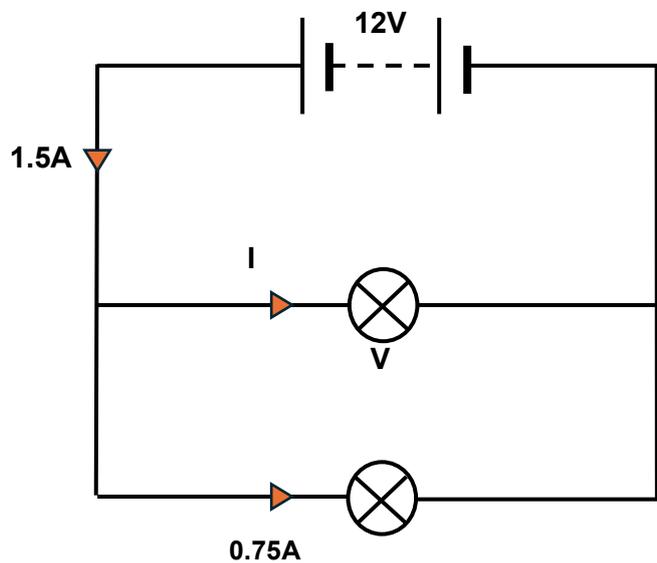
2. What are the values of V and I in this diagram?



$I = \dots\dots\dots$

$V = \dots\dots\dots$

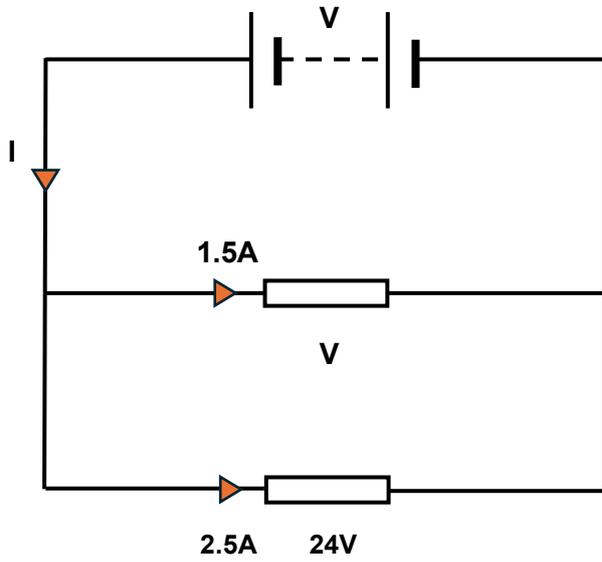
3. This diagram shows 2 different resistors in parallel. What are the values of current I , and voltage V ?



$I = \dots\dots\dots$

$V = \dots\dots\dots$

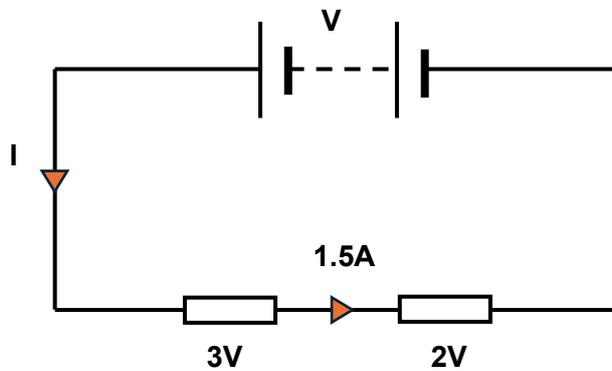
4. This diagram shows 2 different resistors in series. What are the values of current I , and voltage V ?



$I = \dots\dots\dots$


$V = \dots\dots\dots$

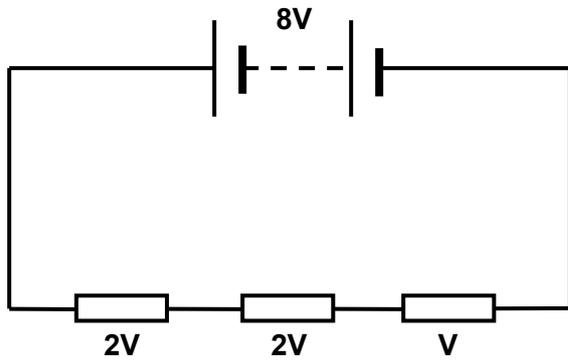5. These resistors may have different values. What is the value of V ?




$V = \dots\dots\dots$

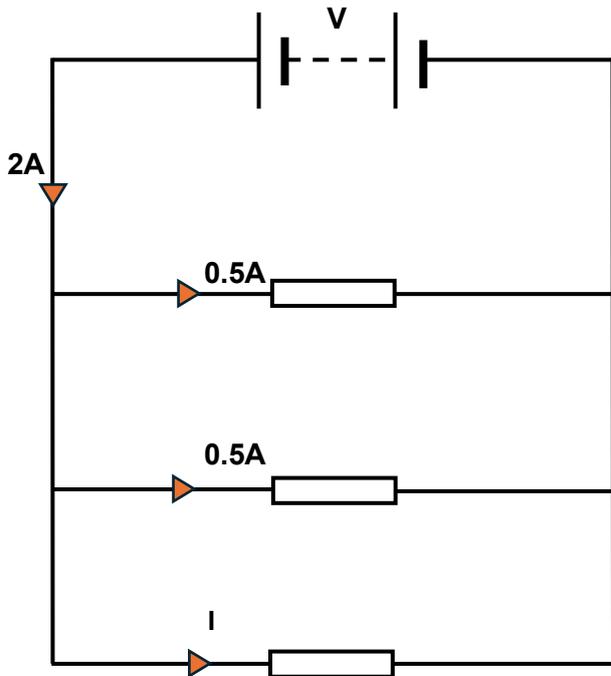6. These resistors may have different values. What is the value of I ?



$I = \dots\dots\dots$

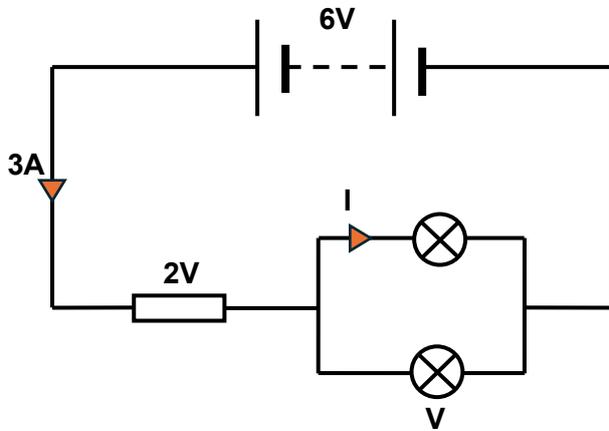
7. The two lamps in this diagram are identical. What are the values of V and I ?



$I = \dots\dots\dots$

$V = \dots\dots\dots$

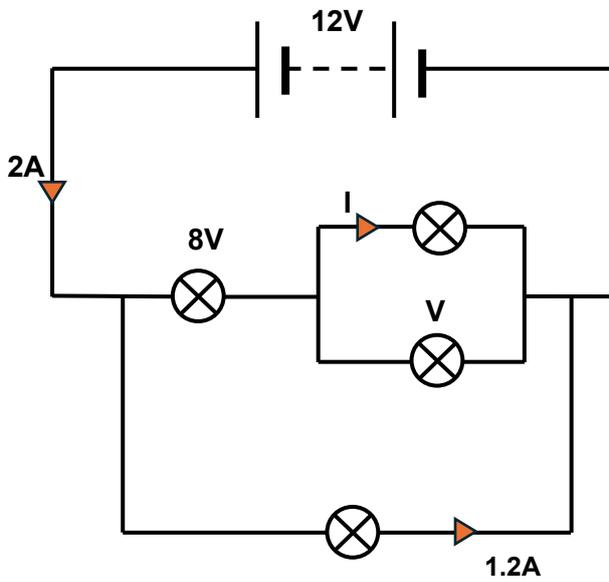8. All the lamps are identical in this circuit. What are the values of I and V ?



$I = \dots\dots\dots$

$V = \dots\dots\dots$